


Memory Elements

Engineering 304

- Latches and Flip-Flops
- Registers
 - VHDL versions
- Shift Registers and Counters
 - VHDL versions


Cross-Coupled NOR Latch

 - Simplest form of memory
- Avoid invalid state
($Q\text{-bar}=Q$)




Gated Latch

 - Cross-Coupled NAND need S and R inverted
- Often SR latches include a control line (Enable)




Level vs. Edge

 - Latches are level-sensitive using Enable input (Q_a)
 - book calls the Enable the “CLK”
- Flip-flops are edge-triggered using Clock input
 - Rising (Q_b) or Falling (Q_c)




Level vs. Edge

 - Latches are level-sensitive using Enable input (Q_a)
 - book calls the Enable the “CLK”
- Flip-flops are edge-triggered using Clock input
 - Rising (Q_b) or Falling (Q_c)




Level vs. Edge

 - Latches are level-sensitive using Enable input (Q_a)
 - book calls the Enable the “CLK”
- Flip-flops are edge-triggered using Clock input
 - Rising (Q_b) or Falling (Q_c)



Level vs. Edge

 - Latches are level-sensitive using Enable input (Q_a)
 - book calls the Enable the "CLK"
- Flip-flops are edge-triggered using Clock input
 - Rising (Q_b) or Falling (Q_c)



Characteristic Table

- Truth Table that includes time aspect ($Q(t) \rightarrow Q(t+1)$)
 - Given certain inputs, what output is expected from the memory device?
- SR
 - D
 - T
 - JK
- An "Excitation Table" lists the required inputs needed to cause a particular output change

Characteristic Tables

SR Latch						JK Flip-Flop					
S	R	Q(t)	Q(t+1)			J	K	Q(t)	Q(t+1)		
0	0	0	0	No Change		0	0	0	0		
0	0	1	1			0	0	1			
0	1	0	0			0	1	0			
0	1	1	0	Reset		0	1	1			
1	0	0	1			1	0	0			
1	0	1	1			1	0	1			
1	1	0	X	Set		1	1	0			
1	1	1	X			1	1	1			
				Invalid							
D Flip-Flop						T Flip-Flop					
D	Q(t)	Q(t+1)				T	Q(t)	Q(t+1)			
0	0					0	0				
0	1					0	1				
1	0					1	0				
1	1					1	1				

Characteristic Tables

SR Latch					JK Flip-Flop			
S	R	Q(t)	Q(t+1)		J	K	Q(t)	Q(t+1)
0	0	0	0	No Change	0	0	0	0
0	0	1	1		0	0	1	1
0	1	0	0		0	1	0	0
0	1	1	0	Reset	0	1	1	0
1	0	0	1		1	0	0	1
1	0	1	1	Set	1	0	1	1
1	1	0	X		1	1	0	1
1	1	1	X	Invalid	1	1	1	0

D Flip-Flop			T Flip-Flop		
D	Q(t)	Q(t+1)	T	Q(t)	Q(t+1)
0	0	0	0	0	0
0	1	0	0	0	1
1	0	1	1	1	0
1	1	1	1	1	1

Excitation Tables

SR Latch				JK Flip-Flop			
Q(t)	Q(t+1)	R	S	Q(t)	Q(t+1)	J	K
0	0	d	0	0	0		
0	1	0	1	0	1		
1	0	1	0	1	0		
1	1	0	d	1	1		

D Flip-Flop			T Flip-Flop		
Q(t)	Q(t+1)	D	Q(t)	Q(t+1)	T
0	0		0	0	
0	1		0	1	
1	0		1	0	
1	1		1	1	

Excitation Tables

SR Latch				JK Flip-Flop			
Q(t)	Q(t+1)	R	S	Q(t)	Q(t+1)	J	K
0	0	d	0	0	0	0	d
0	1	0	1	0	1	1	d
1	0	1	0	1	0	d	1
1	1	0	d	1	1	d	0

D Flip-Flop			T Flip-Flop		
Q(t)	Q(t+1)	D	Q(t)	Q(t+1)	T
0	0	0	0	0	0
0	1	1	0	1	1
1	0	0	1	0	1
1	1	1	1	1	0

VHDL D Flip-Flop

```

ENTITY flipflop IS
  PORT ( D, Resetn, Clock : IN      STD_LOGIC ;
         Q                : OUT     STD_LOGIC );
END flipflop ;
ARCHITECTURE Behavior OF flipflop IS
BEGIN
  PROCESS ( _____ )
  BEGIN
    IF Resetn = '0' THEN
      Q <= '0' ;
    ELSIF Clock'EVENT AND Clock = '1' THEN
      Q <= D ; -- notice there is no "Else" clause
    END IF ;
  END PROCESS ;
END Behavior ;

```

VHDL D Flip-Flop

```

ENTITY flipflop IS
  PORT ( D, Resetn, Clock : IN      STD_LOGIC ;
         Q                : OUT     STD_LOGIC );
END flipflop ;
ARCHITECTURE Behavior OF flipflop IS
BEGIN
  PROCESS ( (Resetn, Clock) )
  BEGIN
    IF Resetn = '0' THEN
      Q <= '0' ;
    ELSIF Clock'EVENT AND Clock = '1' THEN
      Q <= D ; -- notice there is no "Else" clause
    END IF ;
  END PROCESS ;
END Behavior ;

```

Sens. List must be exactly this!

If-elsif must be exactly this!

VHDL n-Bit Register

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY regn IS
  GENERIC ( N : INTEGER := 16 ) ;
  PORT ( D : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
         Resetn, Clock : IN      STD_LOGIC ;
         Q : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END regn ;
ARCHITECTURE Behavior OF regn IS
BEGIN
  PROCESS ( _____ )
  BEGIN
    IF Resetn = '0' THEN
      Q <= (OTHERS => '0') ;
    ELSIF _____ THEN
      Q <= D ;
    END IF ;
  END PROCESS ;
END Behavior ;

```


VHDL n-Bit Register

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY regn IS
    GENERIC ( N : INTEGER := 16 ) ;
    PORT ( D
          : IN  STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
          Resetn, Clock
          : IN  STD_LOGIC ;
          Q
          : OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END regn ;
ARCHITECTURE Behavior OF regn IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= (OTHERS => '0') ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;

```

Flip-Flop Test Bench

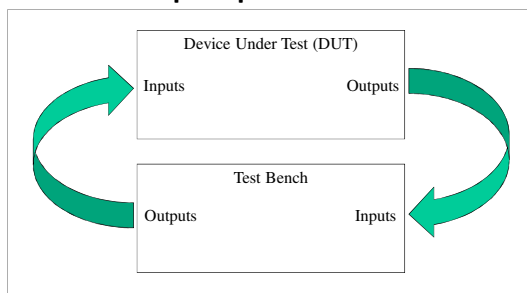

Test Bench Code

```

ENTITY flipflop_TestBench IS
END flipflop_TestBench;
ARCHITECTURE test OF flipflop_TestBench IS
    component flipflop IS port ( -- declare the component
        D, Resetn, Clock : IN STD_LOGIC ;
        Q : OUT STD_LOGIC ) ;
    end component flipflop ;
    signal Dsig : std_logic; -- declare the internal signals
    signal Resetnsig : std_logic;
    signal Clocksig : std_logic;
    signal Qsig : std_logic;
BEGIN
    DUT: flipflop port map ( -- instantiate the flipflop
        D => Dsig, Resetn => Resetnsig, Clock => Clocksig, Q => Qsig
    );

```

Test Bench Code (cont.)

```

process is    -- no sensitivity list => use "wait" instead
begin
  Resetnsig <= '0';
  Clocksig <= '0';
  Dsig <= '1';
  wait for 10 ns; -- reset everything
  assert Qsig = '0' report "Q not reset to zero"
    severity WARNING;
  Resetn <= '1';
  wait for 10 ns; -- reset off, but still Q=0
  assert Qsig = '0' report "Q not staying at zero after reset"
    severity WARNING;
  Clocksig <= '1'; -- rising edge should clock in D=1
  wait for 10 ns; -- let clock edge do something
  assert Qsig = '1' report "Q should now be 1"
    severity WARNING;

```

Test Bench Code (cont.)


```


Dsig <= '0';
wait for 10 ns; -- should be no change when changing D
assert Qsig = '1' report "Q not staying as 1"
  severity WARNING;
Clocksig <= '0';
wait for 10 ns; -- should be no change with falling clk
assert Qsig = '1' report "Q changed on falling clock"
  severity WARNING;
Clocksig <= '1'; -- rising edge
wait for 10 ns; -- D=0 should be clocked in
assert Qsig = '0' report "D=0 not clocked in"
  severity WARNING;
wait; -- never go past this spot - infinite loop-like
end process;
END test;


```

Sequential Devices

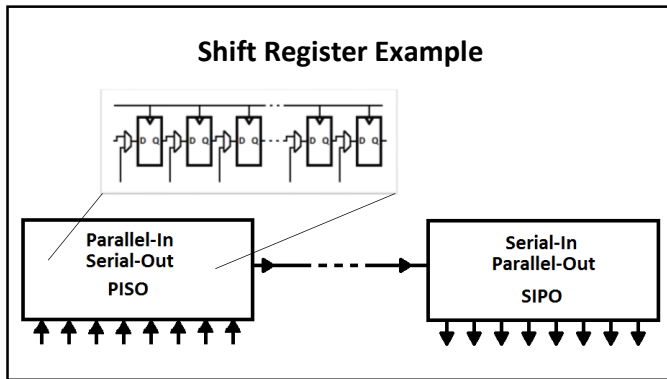
- Registers
 - Shift
 - Parallel In, Serial Out
- Counters
 - Up, down, up/down, modulo-n
 - Ring, Johnson (also shift registers)



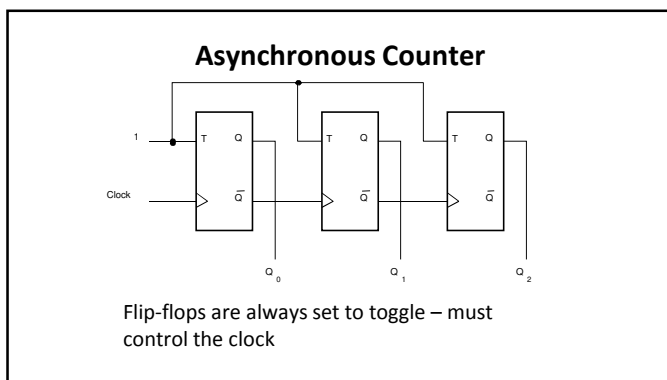

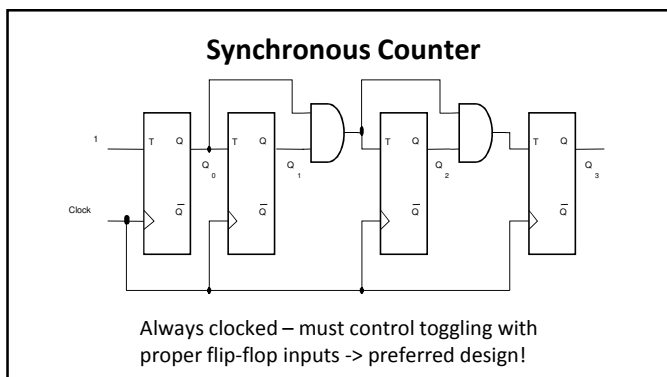


Modulo-n Counters

 

- As soon as count(Q2 Q1 Q0) = then asynchronously clear flip-flops.
 - (5 is never really seen by the user)

Modulo-n Counters

 

- As soon as count(Q2 Q1 Q0) = "1d1" = 5 (or 7), then asynchronously clear flip-flops. (5 is never really seen by the user)
- Also, consider the 001 to 010 transition

Modulo-n Counter

- Asynchronous load or clear
 - Check for trouble with bits changing slightly out of order
- Best practice is to only use asynchronous clearing through the global chip reset

VHDL Enabled Counter

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY upcount IS
    PORT ( Clock, Resetn, E : IN STD_LOGIC ;
          Q : OUT STD_LOGIC_VECTOR (3 DOWNTO 0)) ;
END upcount ;
ARCHITECTURE Behavior OF upcount IS
    SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNTO 0) ;
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN Count <= "0000" ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF E = '1' THEN Count <= Count + 1 ;
            ELSE Count <= Count ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count ; -- finally, assign the output Q from the signal Count
END Behavior ;

```

VHDL Enabled Counter

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY upcount IS
    PORT ( Clock, Resetn, E : IN STD_LOGIC ;
          Q : OUT STD_LOGIC_VECTOR (3 DOWNTO 0)) ;
END upcount ;
ARCHITECTURE Behavior OF upcount IS
    SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNTO 0) ;
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN Count <= "0000" ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF E = '1' THEN Count <= Count + 1 ;
            -- ELSE Count <= Count ; -- not needed as assumed
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count ; -- finally, assign the output Q from the signal Count
END Behavior ;

```

VHDL Modulo-n Counter

```

1 library ieee;
2 use ieee.std_logic_1164.all;
3 use ieee.std_logic_arith.all;
4 use ieee.std_logic_unsigned.all;
5 entity counter_ex is
6     generic ( NUM_BITS : integer := 4; MIN_CNT : integer := 4;
7              MAX_CNT : integer := 13 );
8     port ( CLK, RSTn : IN std_logic;
9           Count : OUT std_logic_vector(NUM_BITS - 1 downto 0) );
10 end entity counter_ex;
11 architecture behave of counter_ex is
12     signal cnt : std_logic_vector(NUM_BITS - 1 downto 0);
13 begin
14     cntr: process (RSTn, CLK) is
15         if (RSTn = '0') then
16             cnt <= conv_std_logic_vector(MIN_CNT, NUM_BITS);
17         elsif (CLK = '1' and CLK'event) then -- rising edge
18             if (cnt = MAX_CNT) then
19                 cnt <= conv_std_logic_vector(MIN_CNT, NUM_BITS);
20             else
21                 cnt <= cnt + 1; -- increment the count
22             end if;
23         end if; -- no else, so inferring a register here
24     end process;
25     Count <= cnt;
26 end architecture behave;

```

VHDL Enabled Counter

```

ARCHITECTURE Behavior OF counter IS
  component counter_ex is
    generic(NUM_BITS : integer := 4; MIN_CNT : integer := 4;
            MAX_CNT : integer := 13);
    port (CLK, RSTn : IN std_logic;
          Count : OUT std_logic_vector((NUM_BITS - 1) downto 0));
  end component counter_ex;
BEGIN
  C0 : component counter_ex
    generic map (NUM_BITS => 4, MIN_CNT => 2, MAX_CNT => 11)
    port map (CLK => my_clock, RSTn => my_reset, Count => Count0);
  C1 : component counter_ex
    generic map (NUM_BITS => 6, MIN_CNT => 3, MAX_CNT => 49)
    port map (CLK => my_clock, RSTn => my_reset, Count => Count1);
  C2 : component counter_ex
    generic map (NUM_BITS => 3, MIN_CNT => 1, MAX_CNT => 7)
    port map (CLK => my_clock, RSTn => my_reset, Count => Count2);
END Behavior ;

```

VHDL Modulo-n Counter - Quartus

