

Block Diagrams

Engineering 304 Lab

Outline

- Overview of uses
- Example DE2 Block Diagram
 - Level 0
 - Level 1
 - Level 2

Why Use Block Diagrams?

- System Engineering is how you design a system with multiple components that interact
 - Much of your work in the future will be a form of system engineering
 - Less focus on the low level components
 - Move focus on how components connect together
- Good tool for communicating your ideas
- Helpful for dividing and conquering a complex design
 - E.g. senior design project

What are the different levels?

- Level 0
 - Identifies system inputs, outputs, and function
- Level 1
 - Identifies primary sub-systems, connections between them, and functionality of each
- Level 2
 - For each primary sub-system, secondary sub-systems are identified.
- Level n
 - Continues until you reach the lowest component level desired
- Example follows for the DE2 board with a NIOS CPU

DE2 Board – Level 0

USB



DE2 Board

Switches



HEX displays




Red LEDs




Keys




DE2 Board – Level 1

 

DE2 Board – Level 2

 

DE2 Board – Level 3 – CPU Only

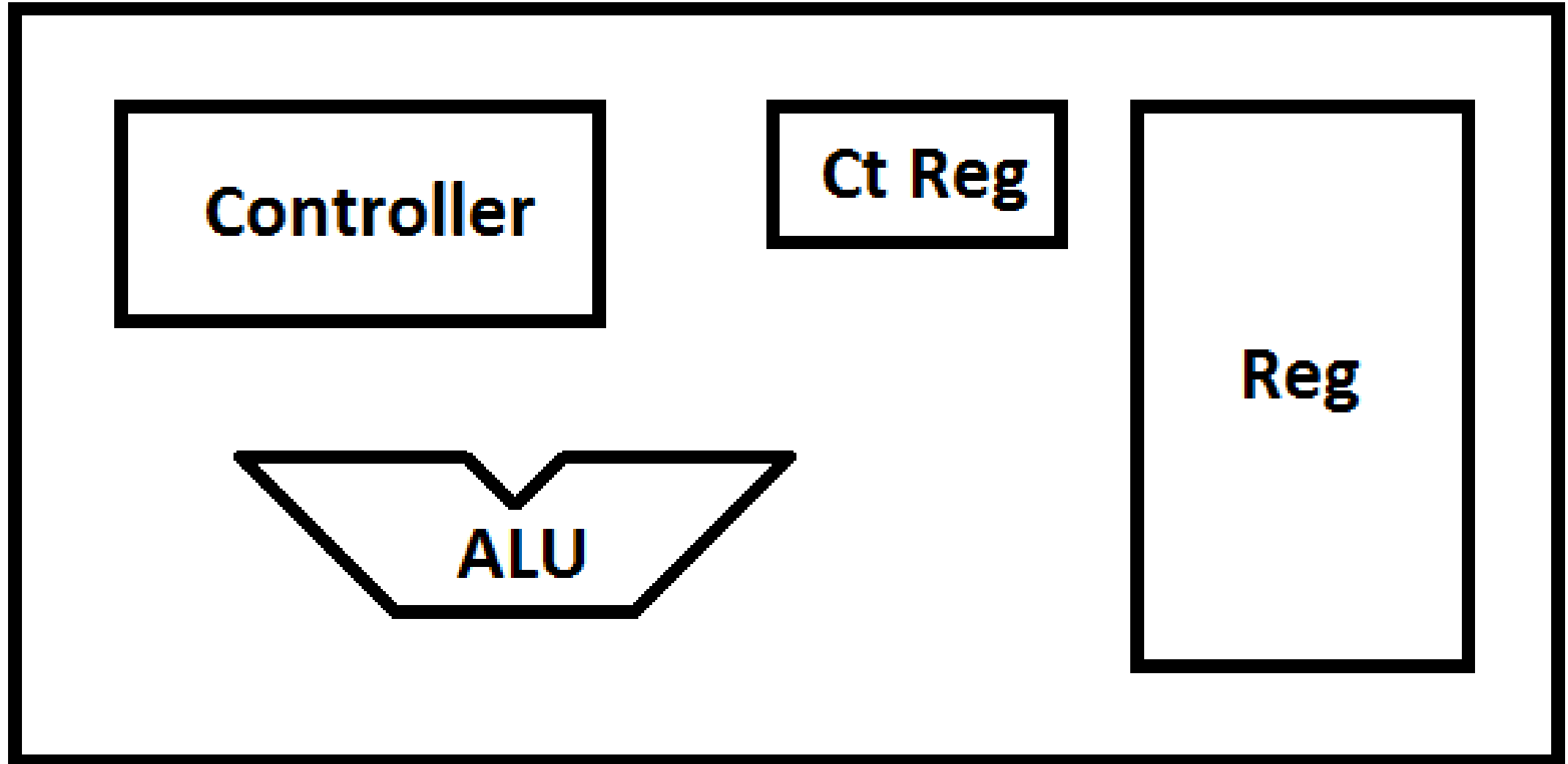


Common Logic Block Symbols



+ logic gate
symbols


VHDL and Block Diagrams

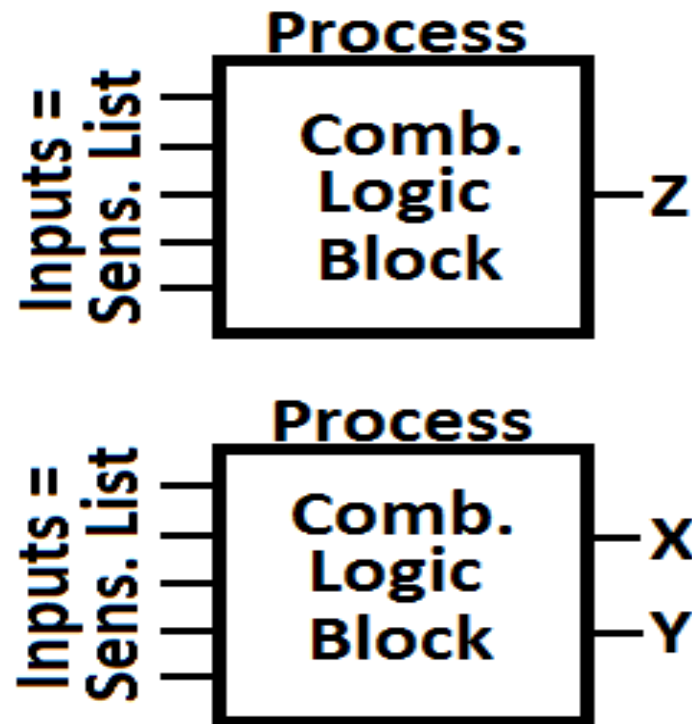- A VHDL process should describe one (or a group) of blocks on your block diagram
- VHDL processes should have only 1 output (or 2 if the two are almost identical)



VHDL and Block Diagrams

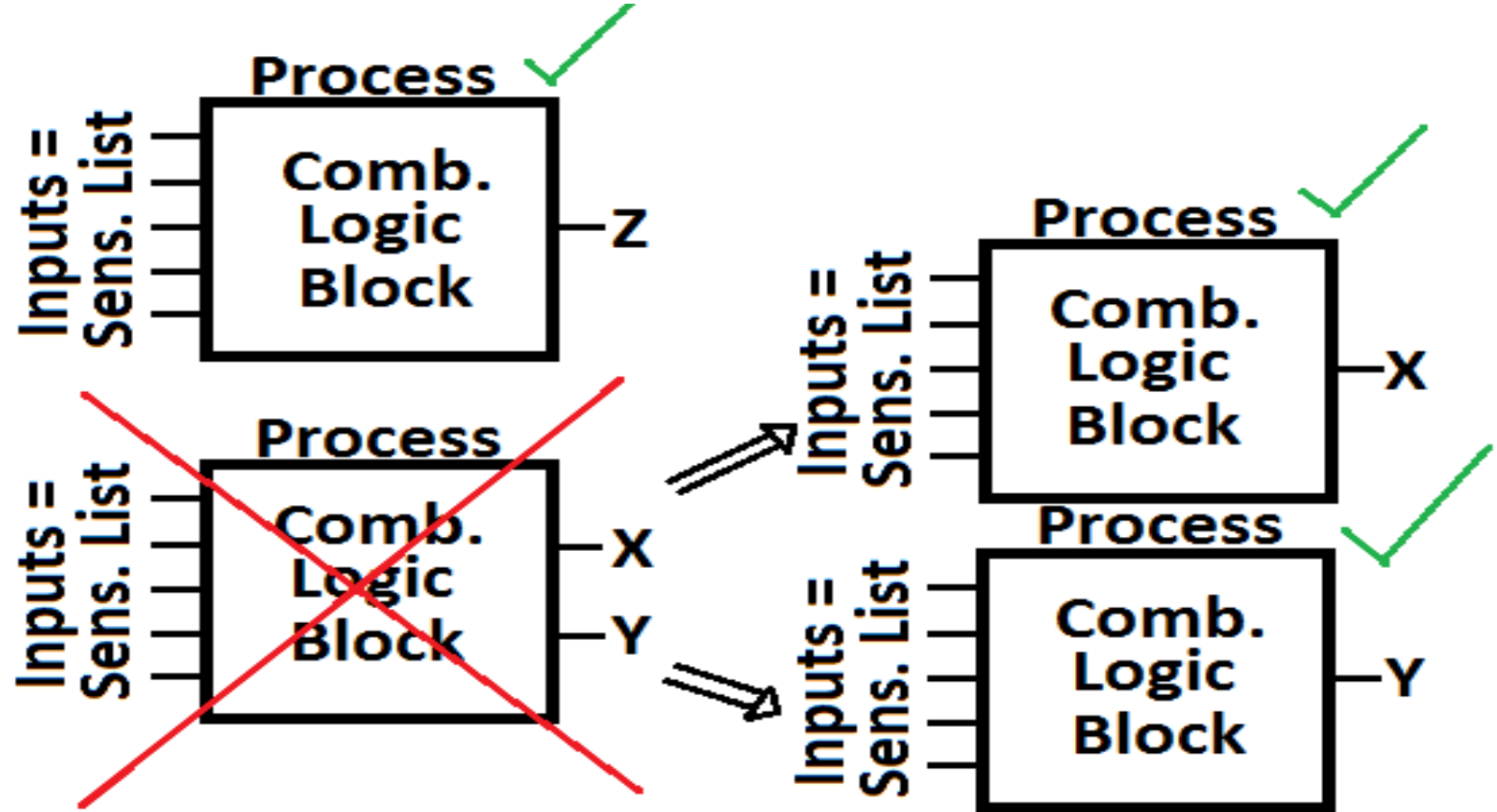- A VHDL process should describe one (or a group) of blocks on your block diagram
- VHDL processes should have only 1 output (or 2 if the two are almost identical)



MUX – Selected Signal Assignment

```
entity Multiplexer is
```

```
    port( A, B, S : IN  BIT ;  
          F       : OUT BIT ) ;
```

```
end Multiplexer ;
```

```
architecture SelectedSignal of Multiplexer is  
begin
```

```
    with S select
```

```
        F <= A when '0',  
           B  when OTHERS ;
```

```
end SelectedSignal ;
```

MUX – Conditional Signal Assignment

```
entity Multiplexer is
```

```
    port( A, B, S : IN  BIT ;  
          F       : OUT BIT ) ;
```

```
end Multiplexer ;
```

```
architecture ConditionalSignal of Multiplexer is  
begin
```

```
    F <= A when S = '0' else  
        B ;
```

```
end ConditionalSignal ;
```

MUX – Process If-Else

```
entity Multiplexer is
    port( A, B, S: IN  BIT ;
          F      : OUT BIT ) ;
end Multiplexer ;
architecture ProcessIfElse of Multiplexer is
begin
    process( A, B, S )
    begin
        if S = '0' THEN
            F <= A ;
        else
            F <= B ;
        end if ;
    end process;
end ProcessIfElse ;
```

MUX – Process Case Statement

```
entity Multiplexer is
    port( A, B, S: IN    BIT ;
          F      : OUT BIT ) ;
end Multiplexer ;
architecture ProcessCase of Multiplexer is
begin
    process( A, B, S )
    begin
        case S IS
            when '0' =>      F <= A ;
            when OTHERS =>    F <= B ;
        end case ;
    end process;
end ProcessCase ;
```